

Coding Boolean

Complete the truth for the AND gate.

Input A	Input B	Input Q
0	0	
0	1	
1	0	
1	1	

Complete the truth for the OR gate.

Input A	Input B	Input Q
0		
0		
1		
1		

Complete the truth for the NOT gate.

Input A	Input B	Input Q
0		
1		